

Sequential Circuit Design

Tom Kelliher, CS 220

Nov. 3, 2001

1 Administrivia

Announcements

Assignment

Read 4-8.

From Last Time

Sequential circuit analysis.

Outline

1. Sequential circuit design process.
2. Unused states.
3. Examples.

Coming Up

VHDL for sequential circuits.

2 Sequential Circuit Design Process

1. Obtain a state diagram. Assign binary numbers to the states (a non-trivial problem, actually).
2. Obtain a state table.
3. Derive flip-flop input equations from the next state entries and output equations. Simplify.
4. Draw your schematic.

3 Unused States

Suppose your design has 6 states:

1. Two unused states.
2. What happens if the circuit enters one of these states?

4 Examples

1. Sequence recognizer for 010.
2. Serial comparator. Inputs: A, B, msb. A and B are received least significant bit first. Receipt of msb is co-incident with msb's of A and B and resets circuit to begin next comparison. Output 0 if $A \geq B$, otherwise 1.
3. Serial comparator. Inputs: A, B, lsb. A and B are received most significant bit first. Receipt of lsb is co-incident with lsb's of A and B and resets circuit to begin next comparison. Output 0 if $A \geq B$, otherwise 1.