

# Counters

Tom Kelliher, CS 220

Nov. 12, 2003

## 1 Administrivia

### Announcements

Exam Friday.

### Assignment

Read 6-1,6 for Monday.

### From Last Time

Shift registers.

### Outline

1. Ripple counters.
2. Synchronous counters.
3. VHDL.

## Coming Up


Memory, ROM.

## 2 Ripple Counters

The increment ripples — propagation delay problems.

Slow counters.

Basic idea:

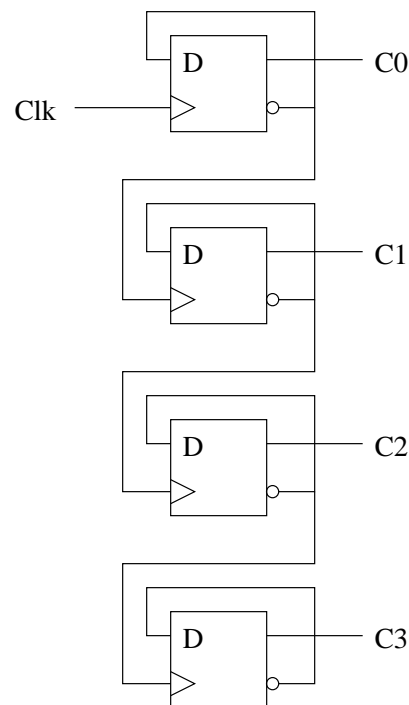


1. Each flip-flop's !Q is fed back to D. What does this accomplish?
2. Flip-flop  $i$ 's !Q is used to clock flip-flop  $i + 1$ . What does this accomplish?
3. Trace the propagation delay of the clock if the count is currently 1111 and a rising clock edge is applied.
4. Through what sequence, starting with 0000, does the counter count?

### 3 Synchronous Counters

1. All flip-flops receive same clock signal.
2. Still have some rippling. (Where?)
3. Inputs: clk, enable.
4. Outputs: count, carry output (for cascading).
5. After state table minimization, input equation for bit  $i$ :

$$C_i \oplus (C_0 \cdot C_1 \cdot \dots \cdot C_{i-1} \cdot EN)$$

6. One bit slice for serial gating:

 

7. Serial vs. parallel gating.

### 4 VHDL

32 bit up counter with enable and reset.

```
-- Up counter with enable and reset
--
-- Note how en must be handled after the flip-flop generating
-- code.
```

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
```

```

entity counter is

    port (
        clk, reset_n, en : in  std_logic;
        q                 : out std_logic_vector (31 downto 0);
        co                 : out std_logic);

end counter;

architecture behavioral of counter is

    signal count : std_logic_vector (31 downto 0);

begin -- behavioral

    q <= count;

    state: process (clk, reset_n)
    begin -- process state
        if reset_n = '0' then
            count <= X"00000000";
        elsif clk'event and clk = '1' then
            if en = '1' then
                count <= count + X"00000001";
            end if;
        end if;
    end process state;

    carry_out: process (count, en)
    begin -- process carry_out
        if count = X"FFFFFFFF" and en = '1' then
            co <= '1';
        else
            co <= '0';
        end if;
    end process carry_out;

end behavioral;

```