

Building a Simple MIPS Datapath

Tom Kelliher, CS 220

Nov. 11, 2011

1 Administrivia

Announcements

Assignment

Read 4.4.

From Last Time

Project day.

Outline

1. Quick introduction to digital logic.
2. Overview of the MIPS implementation.

Coming Up

Completing the datapath.

2 Quick Introduction to Digital Logic


(Register for CS 240 for the complete introduction.)

2.1 Combinational Logic

1. Basic logic gates: Inverter, AND, OR.
2. One bit full adder:
 - (a) From truth table to gates.
 - (b) Multiple bit adders.
3. 2-1 mux:
 - (a) What is it and why do we need it?
 - (b) From truth table to gates.


2.2 Sequential Logic and Examples

1. The clock signal.

 


Sequential elements are *rising edge sensitive*.


2. Clocking registers.

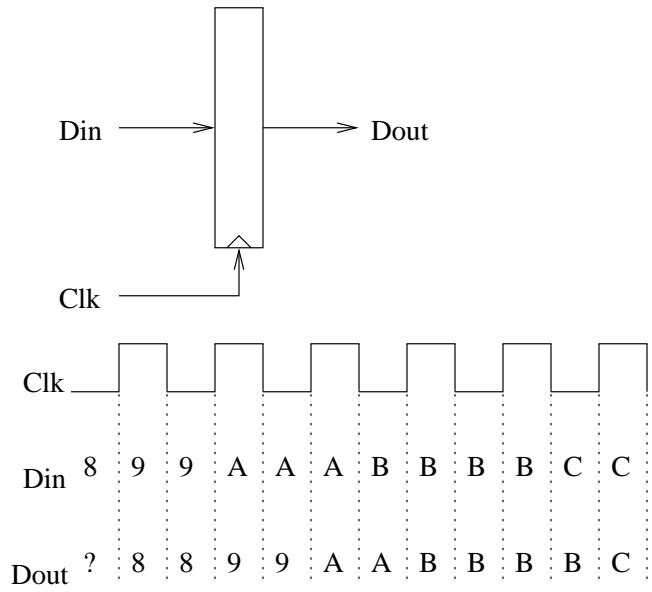


3. A simple pipeline.

 

4. A loadable counter.

 

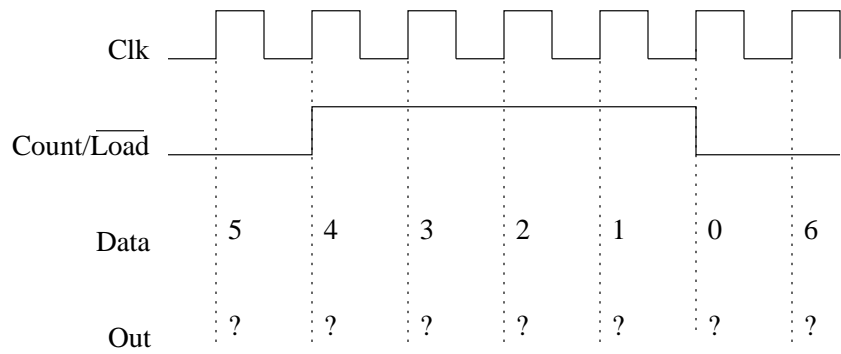

5. Design exercise: four entry register file. Components: loadable register, 4-1 mux, decoder with enable.

3 Overview of the MIPS Implementation

Instruction set subset we'll consider:


1. lw/sw.
2. add, sub, and, or, slt.
3. beq.
4. j.

The general instruction cycle:

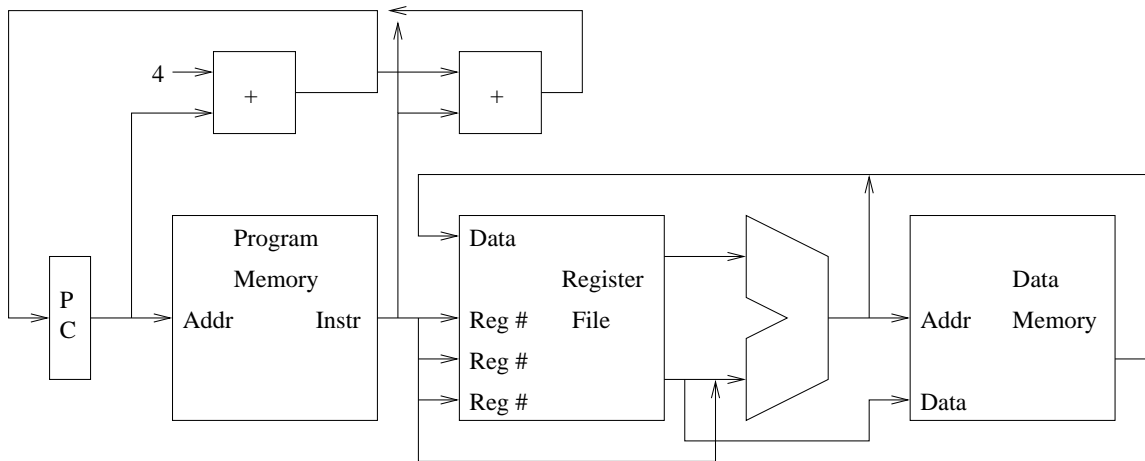1. Instruction fetch.
2. Instruction decode.
3. Register fetch.
4. Operate.
5. Register store or memory operation.

How do the steps of the cycle fit each of the three instruction classes: arithmetic-logic, memory reference, branch?

A high level view of the implementation, in view of the instruction cycle:



1. Datapath only.
2. Is everything we need for our instructions here?
3. Why two memories?