

Counters

Tom Kelliher, CS 220

Apr. 21, 2006

1 Administrivia

Announcements

Where to, next?

Assignment

Read 8-1–5. Don't pay too much attention to ASM diagrams.

From Last Time

Shift registers.

Outline

1. Ripple counters.
2. Synchronous counters.
3. VHDL.

Coming Up


Multiplier

2 Ripple Counters

The increment ripples — propagation delay problems.

Slow counters.

Basic idea:

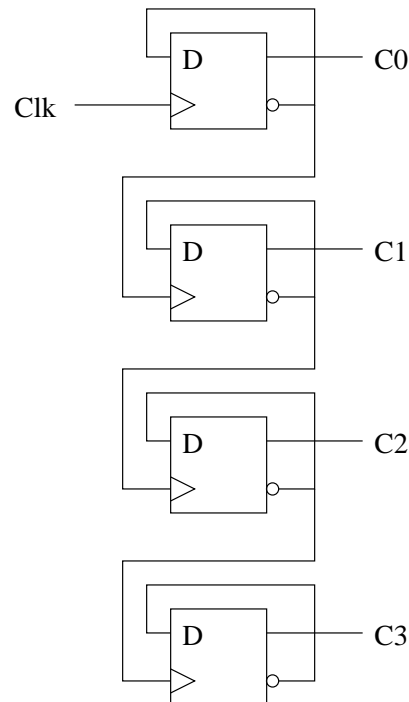


1. Each flip-flop's !Q is fed back to D. What does this accomplish?
2. Flip-flop i 's !Q is used to clock flip-flop $i + 1$. What does this accomplish?
3. Trace the propagation delay of the clock if the count is currently 1111 and a rising clock edge is applied.
4. Through what sequence, starting with 0000, does the counter count?

3 Synchronous Counters

1. All flip-flops receive same clock signal.
2. Still have some rippling. (Where?)
3. Inputs: clk, enable.
4. Outputs: count, carry output (for cascading).
5. After state table minimization, input equation for bit i :

$$C_i \oplus (C_0 \cdot C_1 \cdot \dots \cdot C_{i-1} \cdot EN)$$

6. One bit slice for serial gating:

 

7. Serial vs. parallel gating.

4 VHDL

32 bit up counter with enable and reset.

```
-- Up counter with enable and reset
--
-- Note how en must be handled after the flip-flop generating
-- code.
```

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
```

entity counter is

```
port (  
    clk, reset_n, en : in  std_logic;  
    q                : out std_logic_vector (31 downto 0);  
    co                : out std_logic);
```

end counter;

architecture behavioral of counter is

```
    signal count : std_logic_vector (31 downto 0);
```

begin -- behavioral

```
    q <= count;
```

```
state: process (clk, reset_n)  
begin -- process state  
    if reset_n = '0' then  
        count <= X"00000000";  
    elsif clk'event and clk = '1' then  
        if en = '1' then  
            count <= count + X"00000001";  
        end if;  
    end if;  
end process state;
```

```
carry_out: process (count, en)  
begin -- process carry_out  
    if count = X"FFFFFFFF" and en = '1' then  
        co <= '1';  
    else  
        co <= '0';  
    end if;  
end process carry_out;
```

end behavioral;