# Addition Limits

Tom Kelliher, CS 240  $\,$ 

Feb. 24, 2006

# 1 Administrivia

#### Announcements

Collect assignment.

Assignment

#### From Last Time

Decoders, encoders, muxes.

#### Outline

- 1. A "fast binary adder."
- 2. The lower bound for addition speed.

#### Coming Up

Carry lookahead addition, other integer representations.

## 2 A "Fast Binary Adder"

- 1. Ripple carry adder: example of reuse and divide and conquer.
  - (a) Wire together n full binary adders in order to add two n bit numbers.
  - (b) Running time of a ripple carry adder.Running time of a full binary adder is O(1). Ripple carry adder?Excessive!!!
- 2. An O(1) (!!!) n bit adder.
  - (a) Important equations (briefly explain): Carry generate at bit position *i*:  $G_i = A_i B_i$ . Carry propagate at position *i*:  $P_i = A_i \oplus B_i$ .
  - (b) Carry-in is  $C_0$ .

$$C_1 = G_0 + P_0 C_0.$$
  

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0.$$
  

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0.$$
  
Etc.

- (c) What's the circuit depth of  $C_i$ ?
- (d) What's wrong with this picture?

### 3 The Lower Bound for Addition Speed

- 1. Due to Winograd.
- 2. Our abstract gate for an idealized adder: the (f, r) gate

- (a) Independent of technology.
- (b) f is the fan-in.
- (c) r is the radix (binary).
- (d) Assume that such a gate can compute any r-valued function of f inputs.
- 3. Adding *n* bit numbers. How many inputs? How many outputs? What is the *minimum* number of inputs some output is dependent upon? The *maximum*?
- 4. For the output dependent upon that maximum, consider the ideal circuit which reduces its inputs to the final output.
  - (a) What does it look like?
  - (b) How many intermediate signals remain after one level of gates?
  - (c) What is its depth? That's the lower bound for addition.