

Addition Limits

Tom Kelliher, CS 240

Feb. 20, 2012

1 Administrivia

Announcements

Assignment

From Last Time

Decoders, encoders, muxes.

Outline

1. A “fast binary adder.”
2. The lower bound for addition speed.

Coming Up

Carry lookahead addition, other integer representations.

2 A “Fast Binary Adder”

1. Ripple carry adder: example of reuse and divide and conquer.

(a) Wire together n full binary adders in order to add two n bit numbers.

(b) Running time of a ripple carry adder.

Running time of a full binary adder is $O(1)$. Ripple carry adder?

Excessive!!!

2. An $O(1)$ (!!!) n bit adder.

(a) Important equations (briefly explain):

Carry generate at bit position i : $G_i = A_i B_i$.

Carry propagate at position i : $P_i = A_i \oplus B_i$.

(b) Carry-in is C_0 .

$$C_1 = G_0 + P_0 C_0.$$

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0.$$

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0.$$

Etc.

(c) What's the circuit depth of C_i ?

(d) What's wrong with this picture?

3 The Lower Bound for Addition Speed

1. Due to Winograd.

2. Our abstract gate for an idealized adder: the (f, r) gate

(a) Independent of technology.

(b) f is the fan-in.

- (c) r is the radix (binary).
 - (d) Assume that such a gate can compute any r -valued function of f inputs.
3. Adding n bit numbers. How many inputs? How many outputs? What is the *minimum* number of inputs some output is dependent upon? The *maximum*?
4. For the output dependent upon that maximum, consider the ideal circuit which reduces its inputs to the final output.
- (a) What does it look like?
 - (b) How many intermediate signals remain after one level of gates?
 - (c) What is its depth? — That's the lower bound for addition.