

# Carry Lookahead and Signed-Digit Addition

Tom Kelliher, CS 240

Feb. 27, 2012

## 1 Administrivia

### Announcements

Pay attention!!! A future homework assignment will cover this material, which isn't in the textbook.

### Assignment

Read 4.6–4.7.

### From Last Time

Addition limits.

### Outline

1. Carry lookahead addition.
2. Signed digit representations.

## Coming Up

Introduction to VHDL.

## 2 Carry Lookahead Addition

1. Now, we demonstrate a feasible  $O(\log n)$  adder.


2. Recall:

(a) Carry generate:  $g_i = a_i b_i$ .

(b) Carry propagate:  $p_i = a_i \oplus b_i$ .
 
### 2.1 Carry Lookahead: The Big Picture

Restricting the carry computation circuitry to a tree structure:




- Leaves: Four-bit carry lookahead adders.
- Non-Leaves: Four-bit carry lookahead group units.

### 2.2 Four-Bit Carry Lookahead Adder

1. Design a four-bit full carry lookahead adder.

Block diagram:

 


Block generate, propagate.

2. What is the fan-in?
3. What is the delay model from inputs to outputs?

### 2.3 4-Bit Group Carry Lookahead Unit

1. Design a 4-Group carry lookahead unit.

Block diagram:

 

Use of block generates, propagates.

2. What is the fan-in?
3. What is the delay model from inputs to outputs?

## 2.4 16-Bit Carry Lookahead Adders

Total gate delays for ripple-carry adder.


Gate delays for cascaded and full carry lookahead adders.

## 3 Signed Digit Representations

1. Consider the digit set of the maximally redundant signed digit representation for radix  $r$ :  $\{\overline{r-1}, \overline{r-2}, \dots, \overline{1}, 0, 1, \dots, r-1\}$
2. For radix 2 we have:  $\{\overline{1}, 0, 1\}$ .  
Radix 4:  $\{\overline{3}, \overline{2}, \dots, 3\}$ .
3. For some values, there are multiple representations. For example:  $3 = 011 = 10\overline{1}$  (radix 2).
4. This redundancy can be exploited so that we can design constant time signed digit adders.

### 3.1 Constant Time Radix 2 Signed Digit Adder

 1. Idea: Ensure that a carry propagates no further than two bit positions.
2. Circuit sketch:



3. Stage 1 adder addition table:

| Addend + Augend | Carry | Sum |
|-----------------|-------|-----|
| 2               | 1     | 0   |
| 1               | 1     | 1   |
| 0               | 0     | 0   |
| 1               | 0     | 1   |
| 2               | 1     | 0   |

Goal: Ensure sums are  $\geq 0$  to eliminate -2 as a possible starting sum in the next stage.

4. Stage 2 adder addition table:

| Addend + Augend | Carry | Sum |
|-----------------|-------|-----|
| 1               | 0     | 1   |
| 0               | 0     | 0   |
| 1               | 1     | 1   |
| 2               | 1     | 0   |

Goal: Ensure sums are  $\leq 0$  to eliminate 2 and -2 as possible starting sums in the next stage.

5. Final stage addition table:

| Addend + Augend | Carry | Sum |
|-----------------|-------|-----|
| 1               | 0     | 1   |
| 0               | 0     | 0   |
| 1               | 0     | 1   |