

Project 2: Combinational Chips

CS 220

Start: Sept. 11; Due: Sept. 17 at 11:55 pm

Background

The centerpiece of the computer's architecture is the CPU, or Central Processing Unit, and the centerpiece of the CPU is the ALU, or Arithmetic-Logic Unit. In this project you will gradually build a set of chips, culminating in the construction of the ALU chip of the Hack computer. All the chips built in this project are standard, except for the ALU itself, which differs from one computer architecture to another.

Objective

Build all the chips described in Chapter 2 (see list below), leading up to an Arithmetic Logic Unit - the Hack computer's ALU. The only building blocks that you can use are the chips described in Chapter 1 and the chips that you will gradually build in this project.

Chips

Chip (HDL)	Description	Test script	Compare file
HalfAdder	Half Adder	HalfAdder.tst	HalfAdder.cmp
FullAdder	Full Adder	FullAdder.tst	FullAdder.cmp
Add16	16-bit Adder	Add16.tst	Add16.cmp
Inc16	16-bit incrementer	Inc16.tst	Inc16.cmp
ALU	Arithmetic Logic Unit (without handling of status outputs)	ALU-nostat.tst	ALU-nostat.cmp
ALU	Arithmetic Logic Unit (complete)	ALU.tst	ALU.cmp

Proposed Implementation

As usual, we propose building the chips in the order listed above.

The Hack ALU produces two kinds of outputs: a “main” 16-bit output resulting from operating on the two 16-bit inputs, and two 1-bit “status outputs” named `zr` and `ng`. We recommend building this functionality in two stages. In stage one, implement an ALU that computes and outputs the 16-bit output only, ignoring the `zr` and `ng` status outputs. Once you get this implementation right (that is, once your `ALU.hdl` code passes the `ALU-nostat` test), extend your code to handle the two status outputs as well. This way, any problems detected by `ALU.tst` can be attributed to the incremental code that you've added in stage two. We thank Mark Armbrust for proposing this staged implementation plan, and for supplying the test files to support it.

Contract

When loaded into the supplied Hardware Simulator, your chip design (modified `.hdl` program), tested on the supplied `.tst` script, should produce the outputs listed in the supplied `.cmp` file. If

that is not the case, the simulator will let you know.

Resources

The relevant reading for this project is Chapter 2 and Appendix A. Specifically, all the chips described in Chapter 2 should be implemented in the Hardware Description Language (HDL) specified in Appendix A.

For each chip, we supply a skeletal .hdl file with a missing implementation part. In addition, for each chip we supply a .tst script that instructs the hardware simulator how to test it, and a .cmp (“compare file”) containing the correct output that this test should generate. Your job is to complete and test the supplied skeletal .hdl files.

The resources that you need for this project are the supplied Hardware Simulator and the files listed above. You’ll find the necessary project directory and files in a ZIP file on the course web site.

Tips

Use built-in chips: Your HDL programs will most likely include chip parts that you’ve built in Project 1. As a rule, though, we recommend using the built-in versions of these chips instead. The use of built-in chips ensures correct, efficient, and predictable simulation. There is a simple way to accomplish this convention: make sure that your project directory includes only the .hdl files of the chips developed in the current project.

Implementation order: We recommend building the chips in the order in which they appear in Chapter 2. However, since the simulator features built-in versions of these chips, you can use chip-parts without first building them: the simulator will automatically use their built-in implementations.

Submission and Assessment

If you can’t finish the project on time, submit what you’ve managed to do, and relax. All the projects in this course are highly modular, with incremental test files. Each hardware project consists of many chip modules (*.hdl programs), and each software project consists of many software modules (classes and methods). It is best to treat each project as a modular problem set, and try to work out as many problems as you can. You will get partial credit for partial work.

What if your chip or program is not working? It’s not the end of the world. Hand in whatever you did, and explain what works and what doesn’t in a README file. If you want, you can also supply test files that you developed, to demonstrate working and non-working parts of your project. Instead of trying to hide the problem, be explicit and clear about it. You will get partial credit for your work.

See the next page for the assessment rubric. Submit the following as a single ZIP archive in GoucherLearn:

1. A README file containing the names of all group members. This file may also contain other information, as described above.
2. All your HDL files.
3. Nothing else.

You will lose points for not following these submission instructions.