

A MIPS ALU

Tom Kelliher, CS 240

Feb. 22, 2002

1 Administrivia

Announcements

No class Monday.

Assignment

For Monday, e-mail assembly exercise solution to me. Read 3.10–16.

For Wednesday, read 4.5 — carry lookahead addition.

From Last Time

String handling, summary of addressing modes, program build process.

Outline

1. Building an ALU.


Coming Up

Carry lookahead addition.


2 Building an ALU

Important design principle: reuse.


2-1 mux symbol:

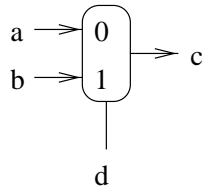

A one-bit two function logical unit:

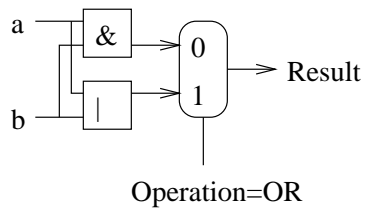


Recall block diagram for full adder:

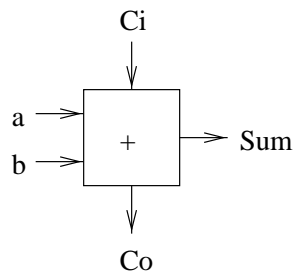


2.1 An ALU

A one-bit three operation ALU:

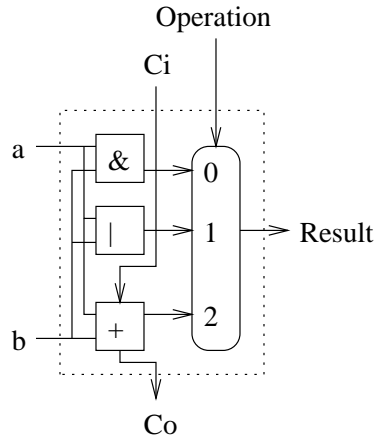

A 32-bit three operation ALU:

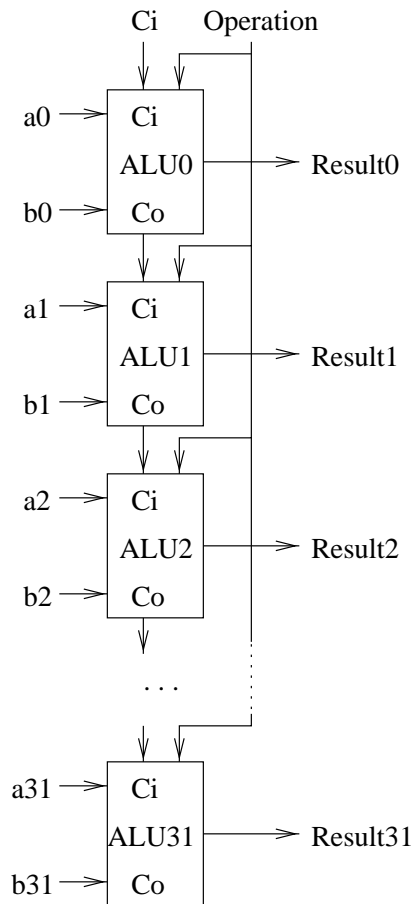

Ripple carry addition.

2.2 A MIPS ALU

What additional functionality needed?

1. Subtraction.
2. `slt` instruction.
3. `beq/bne` comparison.
4. Overflow detection.

How do we modify the basic ALU to handle these operations?

Notes:

1. Semantics of `slt`:

```
slt $t0, $t1, $t2
```

```
$t0 = ($t1 < $t2);
```

2. What is overflow?

- (a) Adding two unsigned numbers.

Can the difference of two unsigned numbers result in an overflow?

- (b) Adding two signed (both positive or both negative) numbers.

Difference?

- (c) Detecting overflow.

2.2.1 Control Summary

Three input lines:

1. Subtract b.
2. Mux select: two lines.
3. Eight possibilities, five used: and, or, add, subtract, set on less than.