

Integrated Circuit Technology

Tom Kelliher, CS 240

Feb. 11, 2008

1 Administrivia

Announcements

Assignment

Read 3.1–2.

From Last Time

NAND gates, two-level implementation, parity.

Outline

1. Terminology.
2. Transmission gates.
3. CMOS.

Coming Up

Combinational logic design process and simulation.

2 Terminology

1. Today's important logic families: TTL, CMOS, LVTTL.

Voltage, current, power, speed.


2. Fan-in, fan-out.
3. Noise margin. Where does noise come from?
4. Power dissipation. Who cares? Extended battery, device life.
5. Propagation delay. Don't forget about wires: on-chip and off-chip.

Delay may be asymmetric: t_{phl} , t_{plh} . Max of both: t_{pd} .


6. We'll only examine *positive logic* and *transport delay*.

3 Transmission Gates


An electronic switch:

 

 Typically used to enable writes onto a bus. For examples, two CPUs sharing a memory bus. Bus arbitration.



 Can be used in more crafty ways: viewing an EXOR as a “conditional inverter:”



Eight transistors; two gate delays.

The standard NAND implementation requires four gates (16 transistors) and has a propagation delay of three gate delays.

4 CMOS

4.1 CMOS Transistors

1. N-type transistor:

(a) Passes GND well.

(b) Degrades Vdd.

(c) Normally open switch.


2. P-type transistor:

(a) Passes Vdd well.

(b) Degrades GND.

(c) Normally closed switch.

Diagrams:

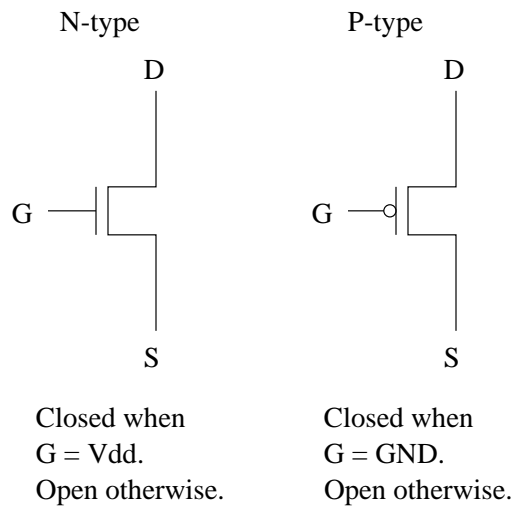


1. Terminals: gate, drain, source.


2. High capacitance on the gate.

4.2 CMOS Logic Gates


A CMOS inverter:

 

A CMOS transmission gate:

 

A CMOS 2-input NAND gate:

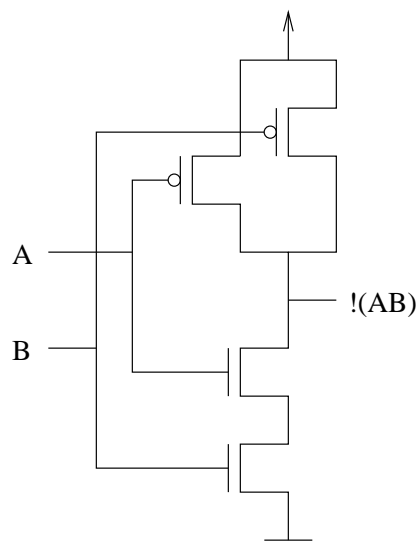

What determines power dissipation? Switching frequency.

Why transport delay isn't a good model: It takes time to move the charge on the gate. This is correctly modeled with inertial delay.