

VHDL for Sequential Circuits

Tom Kelliher, CS 240

Apr. 16, 2010

1 Administrivia

Announcements

Collect assignment; discuss new assignment.

Wednesday's exam covers 4.1–5.2, including material covered in class on addition.

Assignment

Read 7-1–3.

From Last Time

Sequential circuit design.

Outline

1. Modified serial comparator.
2. VHDL for serial comparator.
3. Exercise.

Coming Up

Registers

2 D Flip Flop

Notes:

1. The flip flop's state is maintained by an internal state signal, qInt.
2. The internal state signal drives the q output.
3. Sequential circuitry should never directly drive an output port.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity flipFlop is
    Port ( d      : in std_logic;
           reset   : in std_logic;
           clk     : in std_logic;
           q       : out std_logic);
end flipFlop;

architecture Behavioral of flipFlop is

signal qInt : std_logic;    -- Maintains FF state.

begin

    q <= qInt;    -- Drive FF output from internal state.

    -- Trigger state process if clk OR reset changes.

    state: process (clk, reset)
    begin
        -- Asynchronous active low reset.
        if reset = '0' then
```

```

qInt <= '0';
-- Load new value on rising clock edge.
elsif clk'event and clk = '1' then
    qInt <= d;
end if;
end process state;

end Behavioral;


```

3 Modified Serial Comparator

Inputs: A, B, (no more msb). A and B are received least significant bit first. Output 0 if $A \geq B$, otherwise 1.

Reset to S0 on reset.

State diagram:

 

4 VHDL for Serial Comparator

Things to observe:


1. Flip-flop implementation: reset priority, event, rising edge sensitive.
2. If and case — sequential statements — are valid only within a process.
3. Concurrent assignment is a “process.”
4. Semantics of a process: sensitivity list, assignments:

```
b <= a;
c <= b;
```

does not behave as it would in C.

5. VHDL architecture broken into three processes:

 - (a) State storage.
- (b) Next state generation.
- (c) Output generation.



Compare process inputs to sensitivity lists.

```
-- VHDL for serial comparator. The inputs a and b are input lsb first.
-- The Mealy machine uses rising edge sensitive flip-flops and an
-- asynchronous active low reset.
--
-- The output is 1 if b > a, otherwise 0.
```

```
library ieee;
use ieee.std_logic_1164.all;

entity comparator is
  port
    (a, b, clk, reset : in std_logic;
     o               : out std_logic
    );
```

```

end comparator;

architecture process_defn of comparator is

    -- Two states needed.
    type state_type is (S0, S1);
    -- State assignment.
    attribute enum_encoding : string;
    attribute enum_encoding of state_type :
        type is "0 1";

    signal state, next_state : state_type;

    -- For convenience, concatenate a and b.
    signal inputs : std_logic_vector (1 downto 0);

begin

    -- Concurrent assignment executes the rhs changes.
    -- Concatenate a and b into inputs.
    inputs <= a & b;

    -- Processes execute whenever something on their sensitivity list
    -- changes. All assignments take place when the process exits.
    --
    -- This process implements the D flip-flop.

    state_register : process (clk, reset)
    begin
        -- If/else construct only valid within a process.
        if (reset = '0') then
            state <= S0;
        elsif (clk'event AND clk = '1') then
            state <= next_state;
        end if;
    end process;

    -- This process computes the next state.

    next_state_process : process (inputs, state)
    begin
        case state is

```

```

when S0 =>
    if (inputs = "01") then
        next_state <= S1;
    else
        next_state <= S0;
    end if;

when S1 =>
    if (inputs = "10") then
        next_state <= S0;
    else
        next_state <= S1;
    end if;

end case;
end process;

-- This process computes the output.

output_process : process (inputs, state)
begin
    case state is

        when S0 =>
            if (inputs = "01") then
                o <= '1';
            else
                o <= '0';
            end if;

        when S1 =>
            if (inputs = "10") then
                o <= '0';
            else
                o <= '1';
            end if;

        end case;
    end process;
end process_defn;

```

5 Exercises

1. Serial comparator. Inputs: A, B. A and B are received most significant bit first. Reset to initial state on reset. Output 0 if $A \geq B$, otherwise 1.
2. Serial $3n$ circuit. Design and use D FF and one bit full adder components.