

# Combinational Logic; Hierarchical Design and Analysis

Tom Kelliher, CS 240

Feb. 17, 2010

## 1 Administrivia

### Announcements

Collect assignment.

### Assignment

Read 3.3.

### From Last Time

IC technology.

### Outline

1. Combinational logic.
2. Hierarchical design
3. Design analysis.

## Coming Up


Design example.

## 2 Combinational Logic

1. Definition: Logic circuits in which the output(s) depend solely upon current inputs.
2. No feedback or memory.
3. Sequential circuits: outputs depend upon current inputs *and* previous inputs.

Memory or registers.

4. Example — BCD to 7-segment decoder:

 

## 3 Hierarchical Design

1. Transistor counts:

Device	Count	Year
TI SN7400	16	1966
Intel 4004	2.3 K	1971
Intel 8088	2.9 K	1979
Intel Pentium	3.1 M	1993
Xilinx Virtex	70 M	1997
Intel Pentium 4	42 M	2000
Xilinx Virtex-4	1 B	2004
Sony Cell	241 M	2006
Intel Core 2 Duo	291 M	2006
Intel 6-core Xeon 7400	1.9 B	2008
Altera Stratix IV	2.5 B	2008
AMD HD5800	2.154 B	2009
Intel 8-core Xeon Nehalem-EX	2.3 B	future
NVIDIA GF100	2.9 B	future

2. Design and conquer:

CPU  $\Rightarrow$  Integer Unit  $\Rightarrow$  Adder  $\Rightarrow$  binary full adder  $\Rightarrow$  NAND gates

3. Reuse:

Once logic is collected into a block, it can be instantiated several times in several places.

Adders are used at several points within a CPU: integer ALU, program counter incrementer, multiplier, etc.

Binary full adders are connected to form adders.

4. Scaling:

Consider the two-dimensional tiling of memory cells.

These techniques reduce the number of transistors which must be laid out “by hand.”

Design styles:

1. Top-Down design: divide and conquer.
2. Bottom-Up design: promotes reuse.

The savvy designer often uses both techniques within a single project.

Design tools:

1. CAD tools: programs to assist with schematic capture, HDL entry, synthesis, simulation. Running on “first silicon.”

The “old” days: drafting tables, taping out a circuit, and lots of prototyping.

2. HDLs and synthesis

(a) Why VHDL is my favorite acronym.


(b) What is VHDL? 4-1 mux example:

```
library ieee;
use ieee.std_logic_1164.all;

entity mux4_1 is
    port (a0: in bit;
          a1: in bit;
          d0: in bit;
          d1: in bit;
          d2: in bit;
          d3: in bit;
          z: out bit);
end mux4_1;

architecture behavioral of mux4_1 is
    signal address: bit_vector(1 downto 0);
begin
    address <= a1 & a0;
    with address select
        z <= d0 when "00",
            d1 when "01",
            d2 when "10",
            d3 when "11";
end behavioral;
```

(c) Synthesis process:

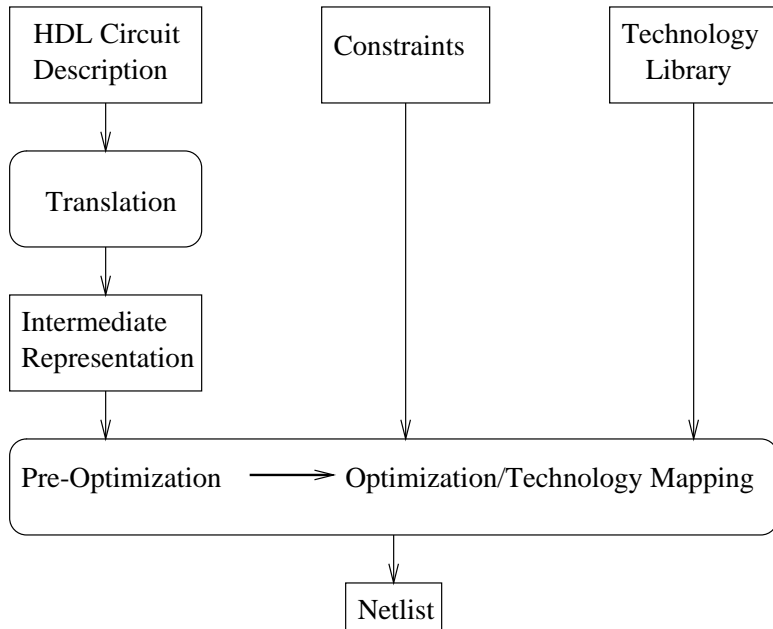

## 4 Design Analysis

Combinational circuit analysis — “reverse engineering.” Skip.

Logic Simulation:

1. Vital today: First silicon must run.

Can’t re-wire a die.

Entire computers have been simulated to the point of booting the OS.

2. Simulator used to verify circuit behavior and timing.

Results are only as good as the tests run.

Large circuits cannot be simulated completely. Just ask Intel (`fdiv`).

3. Netlist used to describe circuit. Text file.

4. Schematic: graphical representation of circuit. Tool to convert to netlist form.

5. User produces “test vectors,” which are the inputs to the simulator.

Good test vectors are the key to meaningful results.