

VHDL for Sequential Circuits

Tom Kelliher, CS 240

Apr. 18, 2012

1 Administrivia

Announcements

Assignment

Read 7-1-3.

From Last Time

Sequential circuit design.

Outline

1. Modified serial comparator.
2. VHDL for serial comparator.
3. Exercise.

Coming Up

Registers

2 D Flip Flop

Notes:

1. The flip flop's state is maintained by an internal state signal, qInt.
2. The internal state signal drives the q output.
3. Sequential circuitry should never directly drive an output port.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity flipFlop is
  Port ( d      : in std_logic;
         reset  : in std_logic;
         clk    : in std_logic;
         q      : out std_logic);
end flipFlop;

architecture Behavioral of flipFlop is

  signal qInt : std_logic;  -- Maintains FF state.

begin

  q <= qInt;  -- Drive FF output from internal state.

  -- Trigger state process if clk OR reset changes.

  state: process (clk, reset)
  begin
    -- Asynchronous active low reset.
    if reset = '0' then
      qInt <= '0';
    -- Load new value on rising clock edge.
    elsif clk'event and clk = '1' then
      qInt <= d;
    end if;
  end process state;
end
```


end Behavioral;

3 Modified Serial Comparator

Inputs: A, B, (no more msb). A and B are received least significant bit first. Output 0 if $A \geq B$, otherwise 1.

Reset to S0 on reset.

State diagram:

 

4 VHDL for Serial Comparator

Things to observe:

1. Flip-flop implementation: reset priority, event, rising edge sensitive.
2. If and case — sequential statements — are valid only within a process.
3. Concurrent assignment is a “process.”
4. Semantics of a process: sensitivity list, assignments:

```
b <= a;  
c <= b;
```


does not behave as it would in C.

5. VHDL architecture broken into three processes:

(a) State storage.

(b) Next state generation.

(c) Output generation.

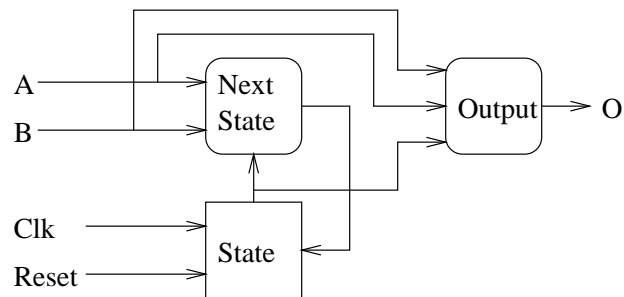

Compare process inputs to sensitivity lists.

```
-- VHDL for serial comparator. The inputs a and b are input lsb first.
-- The Mealy machine uses rising edge sensitive flip-flops and an
-- asynchronous active low reset.
--
-- The output is 1 if b > a, otherwise 0.
```

```
library ieee;
use ieee.std_logic_1164.all;

entity comparator is
    port
        (a, b, clk, reset : in std_logic;
         o                 : out std_logic
        );
end comparator;
```

```
architecture process_defn of comparator is
```

```
-- Two states needed.
```

```

type state_type is (S0, S1);
-- State assignment.
attribute enum_encoding : string;
attribute enum_encoding of state_type :
    type is "0 1";

signal state, next_state : state_type;

-- For convenience, concatenate a and b.
signal inputs : std_logic_vector (1 downto 0);

begin

-- Concurrent assignment executes the rhs changes.
-- Concatenate a and b into inputs.
inputs <= a & b;

-- Processes execute whenever something on their sensitivity list
-- changes. All assignments take place when the process exits.
--
-- This process implements the D flip-flop.

state_register : process (clk, reset)
begin
    -- If/else construct only valid within a process.
    if (reset = '0') then
        state <= S0;
    elsif (clk'event AND clk = '1') then
        state <= next_state;
    end if;
end process;

-- This process computes the next state.

next_state_process : process (inputs, state)
begin
    case state is

        when S0 =>
            if (inputs = "01") then
                next_state <= S1;
            else
                next_state <= S0;
            end if;
    end case;
end process;

```

```

        end if;

    when S1 =>
        if (inputs = "10") then
            next_state <= S0;
        else
            next_state <= S1;
        end if;

    end case;
end process;

-- This process computes the output.

output_process : process (inputs, state)
begin
    case state is

        when S0 =>
            if (inputs = "01") then
                o <= '1';
            else
                o <= '0';
            end if;

        when S1 =>
            if (inputs = "10") then
                o <= '0';
            else
                o <= '1';
            end if;

    end case;
end process;

end process_defn;

```

5 Exercises

1. Serial comparator. Inputs: A, B. A and B are received most significant bit first. Reset to initial state on reset. Output 0 if $A \geq B$, otherwise 1.
2. Serial $3n$ circuit. Design and use D FF and one bit full adder components.